


**Question 1 (25 P)**

List the 4 or 5 (different) application fields of Operational Amplifier. You should use circuit diagrams, diagrams, keywords, ...

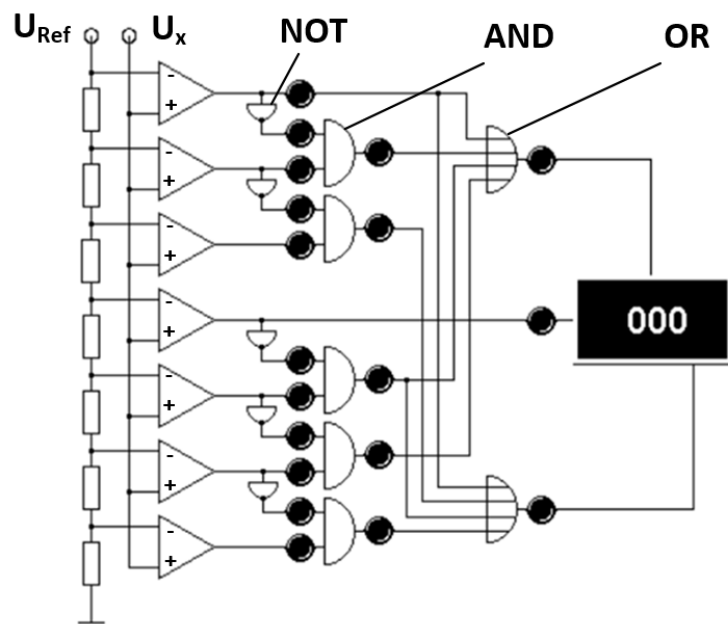**Question 2 (25 P)**

The scheme right shows an Analog-Digital-Converter.


- Give the detailed name
- Describe short in keywords the function and the advantages and the downsides
- For  $U_{Ref} = 14\text{ V}$  and  $U_x = 6.8\text{ V}$  write near the dark black points the signal states „0“ or „1“
- Give the result of the conversation as a digital number.



Note: The devices with + / - are comparators. If  $U_+ > U_-$ , they show the result "1", in the other case they give "0".

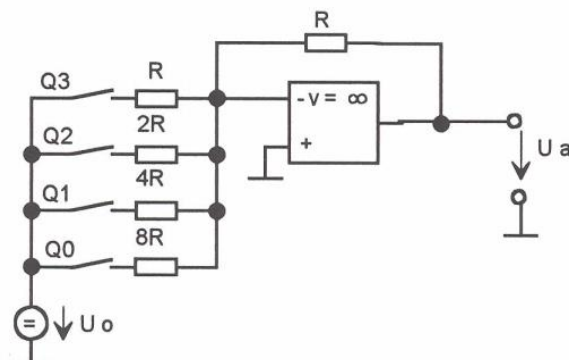**Question 3 (25 P)**

- Describe in keywords the function of the circuit diagram right. How does it work?
- Which voltage has  $U_a$ , if Q3 and Q2 are "on" and Q1 and Q0 are "off". The voltage  $U_0 = 10\text{ V}$ .
- Sketch (parallel) a simplified circuit diagram without the switches with regard to b).





**Question 4 (30 P)**

I) Sketch

- a) the symbols
- b) V-I-diagrams

of a A) diode and B) a Zener diode

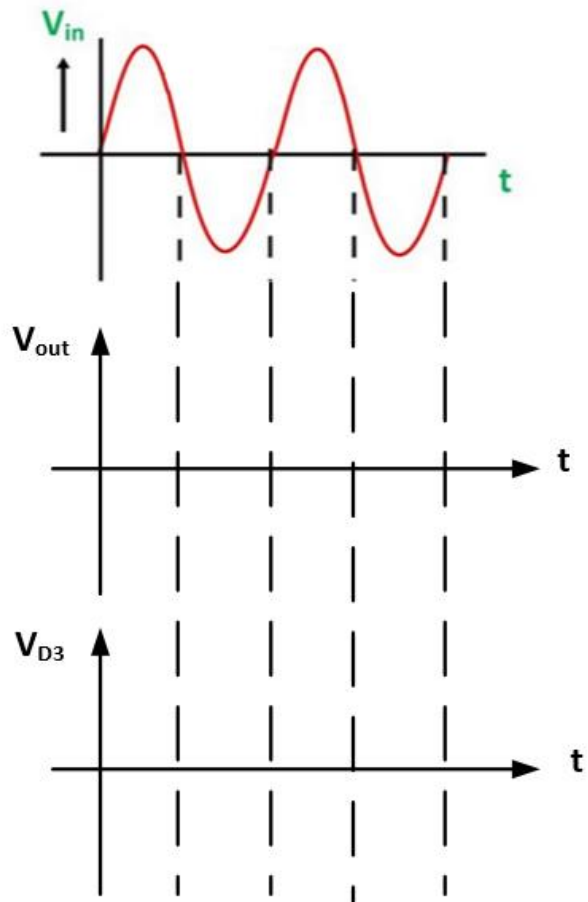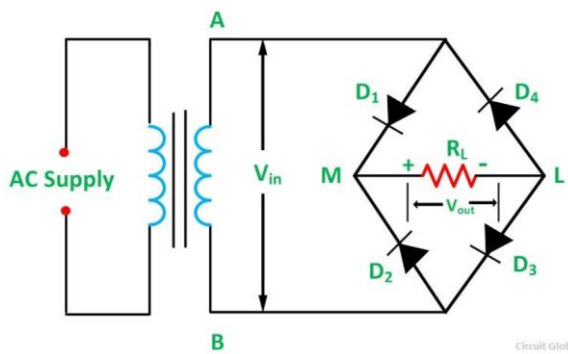II) Given is a full bridge rectifier, see right  
Sketch  $V_{out}$ ,  $V_{D3}$



**Question 5 (15 P)**

You see electronic devices 78xx and 79xx.

- a) What is it?
- b) For what stands xx?
- c) What is the difference between them?
- d) Sketch a principle circuit